 



Problem 3

Determine V_{outq} and $V_{out}(t)$ if $V_{in} = 0.75\sin(500t)$. Assume $\beta=100$ and $V_{dd} = 10V$ with $R_b = 150k\Omega$ $R_c = 1k\Omega$.




Problem 4

Determine V_{outq} and $V_{out}(t)$ if $V_{in} = 2 \sin(500t)$. Assume the AMI06 process and $V_{dd} = 10V$, $V_{ss}= 5V$ with $R_b = 150k\Omega$ $R_c = 2k\Omega$.

 


Problem 5

Given the following two circuits, with $\beta=100$, the MOSFET has a μCOX of 56.4×10^{-6} and $\frac{W}{L} = 1$ with $V_T = 0.71V$. $R_b = 100k\Omega$ and $R_c = 150\Omega$ for the BJT and $5k\Omega$ for the MOSFET, find V_{dd} for each circuit such that their gain is the same (for the MOS you have control of V_{SS} as well). Comment on how much the circuits differ and what changes to get the gain the same.

 

Problem 6

Draw out the two-port Thevenin equivalent amplifier for the following circuit. Equate the different parameters between the small signal circuit and the amplifier you drew out. After that, find R_{in} , R_{out} and A_v for the amplifier. Explain how you found each value (**do not** just restate the final relationships).

 


Problem 7

For the following array of amplifiers, note the output at each step as well as at V_{out} for the following values given $V_{in} = 5V$ and $R_s = 100k\Omega$ and $R_L = 5k\Omega$. At each step comment on the impact of R_{in} and R_{out} of each amplifier. What would be the ideal output of the array? Is it different from your calculations? Why? (try not to round too much so you get a better idea of possible differences).

Amp 1: $A_v = 100$; $R_{in} = \infty$; $R_{out} = 1\Omega$;


Amp 2: $A_v = \frac{1}{200}$; $R_{in} = 100k\Omega$; $R_{out} = 500\Omega$;

Amp 3: $A_v = 2$; $R_{in} = 50k\Omega$; $R_{out} = 1k\Omega$;

 


Problem 8

The below circuit is shown in the small-signal domain. Assume that the circuit is biased such that the MOSFET is operating in the saturation region. Derive the small-signal gain of the circuit. Assume $\lambda = 0$.

 


Problem 9

Derive (do not simply restate) the small-signal input impedance of the common-gate amplifier shown below. If necessary, you may assume that $\lambda = 0$.

 

 Problem 10

Derive (do not simply restate) the small-signal output impedance of the common-gate amplifier shown below. If necessary, you may assume that $\lambda = 0$.




Problem 11 & 12


BJT review

For this problem, assume that β is 100. Remember that $I_E = I_B + I_C$ is true in all operating regions.

 
a) Find V_{OUT} for $V_{IN} = 1V$, $1.5V$, and $2V$. For each V_{IN} , state and prove what region the BJT is in.



 b) For this second circuit, the emitter is no longer grounded. So, in forward active, V_B is no longer 0.6, instead it is $V_E + 0.6V$. Find V_{out} again for $V_{in} = 1V$, $1.5V$, and $2V$.



 c) For this third circuit, an additional device has been added. Note that I_1 is **NOT** I_{C1} since current can also go through the base of device 2, if it is active. Find V_{out} when $V_{in} = 1V$, $1.5V$, and $2V$.



MOSIS WAFER ACCEPTANCE TESTS

RUN: T6AU
TECHNOLOGY: SCN05
microns

VENDOR: AMIS
FEATURE SIZE: 0.5

Run type: SKD

INTRODUCTION: This report contains the lot average results obtained by MOSIS from measurements of MOSIS test structures on each wafer of this fabrication lot. SPICE parameters obtained from similar measurements on a selected wafer are also attached.

COMMENTS: American Microsystems, Inc. C5

TRANSISTOR PARAMETERS	W/L	N-CHANNEL	P-CHANNEL	UNITS
MINIMUM	3.0/0.6			
Vth		0.79	-0.92	volts
SHORT	20.0/0.6			
Idss		446	-239	uA/um
Vth		0.68	-0.90	volts
Vpt		10.0	-10.0	volts
WIDE	20.0/0.6			
Ids0		< 2.5	< 2.5	pA/um
LARGE	50/50			
Vth		0.68	-0.95	volts
Vjbkd		10.9	-11.6	volts
Ijlk		<50.0	<50.0	pA
Gamma		0.48	0.58	V^0.5
K' (Uo*Cox/2)		56.4	-18.2	uA/V^2
Low-field Mobility		463.87	149.69	cm^2/V*s

COMMENTS: Poly bias varies with design technology. To account for mask bias use the appropriate value for the parameter XL in your SPICE model card.

Design Technology	XL (um)	XW (um)
-----	-----	-----
SCMOS_SUBM (lambda=0.30)	0.10	0.00
SCMOS (lambda=0.35)	0.00	0.20

FOX TRANSISTORS	GATE	N+ACTIVE	P+ACTIVE	UNITS
Vth	Poly	>15.0	<-15.0	volts

PROCESS PARAMETERS	N+	P+	POLY	PLY2_HR	POLY2	M1	M2	UNITS
Sheet Resistance	83.5	105.3	23.5	999	44.2	0.09	0.10	
ohms/sq								
Contact Resistance	64.9	149.7	17.3		29.2		0.97	ohms
Gate Oxide Thickness	142							

angstrom

PROCESS PARAMETERS	M3	N\PLY	N_W	UNITS
Sheet Resistance	0.05	824	816	ohms/sq
Contact Resistance	0.79			ohms

COMMENTS: N\POLY is N-well under polysilicon.

CAPACITANCE PARAMETERS	N+	P+	POLY	POLY2	M1	M2	M3	N_W	UNITS
Area (substrate)	425	731	84		27	12	7	37	
aF/um^2									
Area (N+active)			2434		35	16	11		
aF/um^2									
Area (P+active)			2335						
aF/um^2									
Area (poly)				938	56	15	9		
aF/um^2									
Area (poly2)					49				
aF/um^2									
Area (metall)						31	13		
aF/um^2									
Area (metal2)							35		
aF/um^2									
Fringe (substrate)	344	238			49	33	23		aF/um
Fringe (poly)					59	38	28		aF/um
Fringe (metall)						51	34		aF/um
Fringe (metal2)							52		aF/um
Overlap (N+active)			232						aF/um
Overlap (P+active)			312						aF/um

CIRCUIT PARAMETERS			UNITS
Inverters	K		
Vinv	1.0	2.02	volts
Vinv	1.5	2.28	volts
Vol (100 uA)	2.0	0.13	volts
Voh (100 uA)	2.0	4.85	volts
Vinv	2.0	2.46	volts
Gain	2.0	-19.72	
Ring Oscillator Freq.			
DIV256 (31-stg,5.0V)		95.31	MHz
D256_WIDE (31-stg,5.0V)		147.94	MHz
Ring Oscillator Power			
DIV256 (31-stg,5.0V)		0.49	uW/MHz/gate
D256_WIDE (31-stg,5.0V)		1.01	uW/MHz/gate

COMMENTS: SUBMICRON